

1) SR Flip Flop using T Flip flop

Truth Table of SR Flip-flop

Inputs		Outputs	
S	R	Present State Q_n	Next State Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1		invalid
1	1		invalid

Excitation Table of T Flip-flop

Outputs		Input
Present State Q_n	Next State Q_{n+1}	
0	0	0
0	1	1
1	0	1
1	1	0

T to SR Conversion Table

SR Inputs		Outputs		T Input
S	R	Present State Q_n	Next State Q_{n+1}	
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1		invalid	X
1	1		invalid	X

Karnaugh Map for T input:

S \ R	Q_n			
	00	01	11	10
0	0	0	1	0
1	1	0	X	X

$$T = \bar{S}Q_n + RQ_n$$

2) SR Flip flop using JK Flip Flop

Truth Table of SR Flip-flop

Inputs		Outputs	
S	R	Present State Q_n	Next State Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1		invalid
1	1		invalid

Excitation Table of JK Flip-flop

Outputs		Inputs	
Present State Q_n	Next State Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

SR to JK Conversion Table

SR Inputs		Outputs		JK Inputs	
S	R	Present State Q_n	Next State Q_{n+1}	J	K
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	X	1
1	0	0	1	1	X
1	0	1	1	X	0
1	1		invalid	X	X
1	1		invalid	X	X

Karnaugh Map for J input:

S \ R	Q_n			
	00	01	11	10
0	0	X	X	0
1	1	X	X	X

$$J = S$$

Karnaugh Map for K input:

S \ R	Q_n			
	00	01	11	10
0	X	0	1	X
1	X	0	X	X

$$K = R$$